

Roll No. 2021218213

Total Pages : 03

BT-3/D-23

43140

DIGITAL ELECTRONICS

ES-207A

Time : Three Hours]

[Maximum Marks : 75

Note : Attempt *Five* questions in all, selecting at least *one* question from each Unit. All questions carry equal marks.

Unit I

1. (a) Differentiate between the following : 5
 - (i) Positive and negative logic
 - (ii) Positive and negative logic.
- (b) List various logic operations. Mention gates corresponding to them. Explain, how NAND gate can be used to perform OR operation. 5
- (c) Convert decimal numbers into BCD (i) 46, (ii) 327.89, (iii) 20.30. 5
2. (a) State and prove (i) Duality Theorem (ii) De-Morgan's theorem. 5

(5-41/10)L-43140

P.T.O.

- (b) Write the rules of minimization using K-Map. Minimize the given expression using K-Map :
 $F(A, B, C, D) = \Sigma(1, 2, 4, 5, 7, 8, 9, 11, 13, 14)$.
Realise the obtained expression using logic gates.

10

Unit II

3. (a) Draw logic diagram of full adder. Explain its working. 8
(b) Design an octal to binary encoder. 7
4. (a) What is a multiplexer ? Explain working of an $n : 1$ multiplexer. 8
(b) Design a 4 bit comparator. 7

Unit III

5. (a) Differentiate between the following : 5
(i) Latch and flip-flop
(ii) Level triggering and edge triggering.
- (b) Explain working of JK flip-flop. Discuss race around problem of JK flip-flop. Also describe how Master-Slave flip-flop overcomes this problem. 10
6. (a) Explain application of shift register as ring counter. 5
(b) Design a synchronous mode 5 counter. Use JK flip-flops for designing the counter. 10

Unit IV

7. Explain working of the following : **10**
- (i) R-2R ladder type DAC
 - (ii) Successive Approximation type ADC.
8. (a) Draw diagram of a memory cell. Explain either read OR write operation with timing waveforms in memory cell. **10**
- (b) Write a note on ROM. **5**