

Roll No.

Total Pages : 03

GSE/D-22

1164

LOGICAL ORGANIZATION OF
COMPUTER-I
BCA-114

Time : Three Hours]

[Maximum Marks : 80

Note : Attempt *Five* questions in all. Q. No. 1 is compulsory.
Attempt *four* more questions, selecting *one* question
from each Unit. All questions carry equal marks.

1. Answer the following questions in brief :

- (a) What is Radix ? What are digits of hexadecimal number system ? 2
- (b) Represent 'A' in ASCII and EBCDIC codes. 2
- (c) What is principle of duality ? Explain. 2
- (d) State DeMorgan's laws. 2
- (e) What is XOR gate ? Draw truth table and symbol. 2
- (f) What is AND gate ? Draw truth table and symbol. 2
- (g) What is Multiplexer ? Draw the diagram for 4×1 multiplexer and explain its working. 4

(5-20/6) L-1164

P.T.O.

Unit I

2. (a) Convert $(37.23)_{10}$ into binary and hexadecimal number systems. 8
- (b) Add $(9)_{10}$ and $(-14)_{10}$ in two's complement form. 8
3. (a) What are BCD codes ? Write self-complementing and cyclic BCD codes. 8
- (b) What are error detecting and correcting code ? Explain with an example. 8

Unit II

4. (a) State the postulates of Boolean algebra. 8
- (b) Prove the following Boolean theorems using Boolean postulates : 8
- (i) $X + X.Y = X$
- (ii) $X + 1 = 1.$
5. (a) What are canonical representation of Boolean functions ? Explain POS and SOP form of representation with examples. 8
- (b) Simplify the following Boolean function using K-map : 8
- $F(a, b, c, d) = \Sigma (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14).$

Unit III

6. (a) What are NAND and NOR gates ? Why are these called as universal gates ? Explain. 8

L-1164

- (b) Implement $F = A.B + C.D + E$ using NAND logic only. 8
7. (a) What is combinational logic ? What are characteristics of combinational circuits ? Also discuss design procedure of combinational circuits. 8
- (b) What is analysis procedure ? Explain with an example. 8

Unit IV

8. (a) What is full adder ? Design full adder circuit. 8
- (b) What is comparator circuit ? Design 3-bit comparator circuit. 8
9. (a) What is demultiplexer ? Design 1×4 demultiplexer circuit. 8
- (b) Design a circuit to convert 8421 BCD code into excess-3 BCD code. 8